
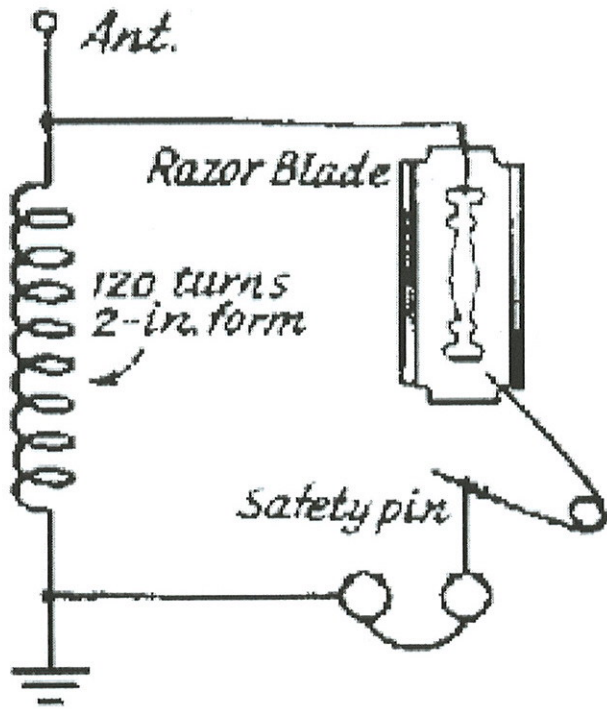


Crystal Radio

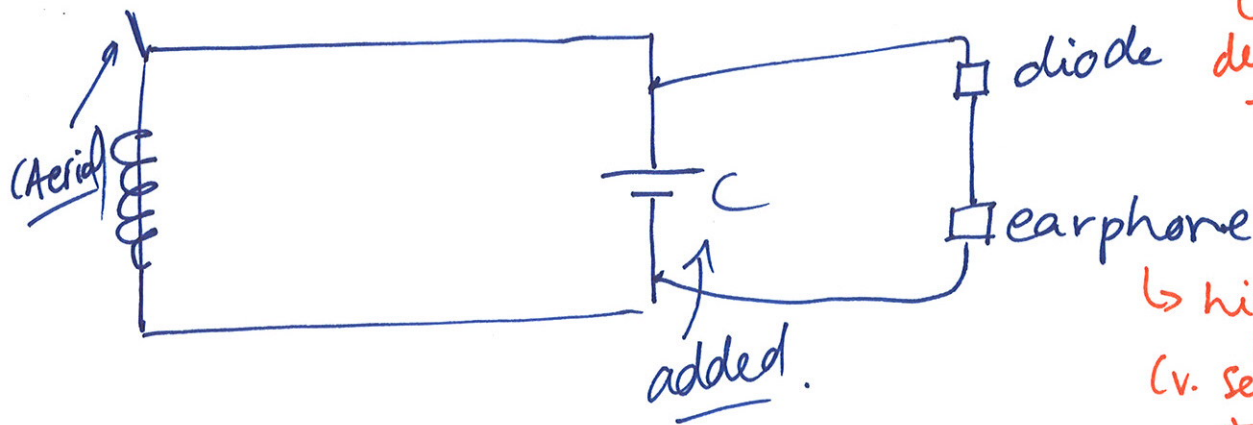

Fox Hole Radio

(<http://www.wikihow.com/Make-a-Crystal-Radio>)



"Crystal" detector, used to be galena.

↳ high-impedance
(v. sensitive to voltage change)

$$LQ'' + \frac{1}{C}Q = \underbrace{A \cos \beta t}$$

RF signal, assume ~~single~~ single-freq.

Solving:

$$Q = \underbrace{C_1 \sin\left(\frac{1}{\sqrt{CL}} t\right) + C_2 \cos\left(\frac{1}{\sqrt{CL}} t\right)}_{\text{homog. sol.}} + \underbrace{\frac{A}{L\left(\frac{1}{CL} - \beta^2\right)}}_{\text{part. sol.}} \cos(\beta t)$$

Let $\omega = \frac{1}{\sqrt{CL}}$ (natural frequency).

Coefficient $\frac{A}{L(\omega^2 - \beta^2)}$. A small
 . coeff gets big as
 $\omega \rightarrow \beta$.


What if $\omega^2 = \beta^2$?

Resonance \rightarrow forcing frequency matches the natural frequency.

ODE: $Q'' + \beta^2 Q = \frac{A}{L} \cos \beta t$ (tuned ω).
 (so $\omega = \beta$)

Particular solution:
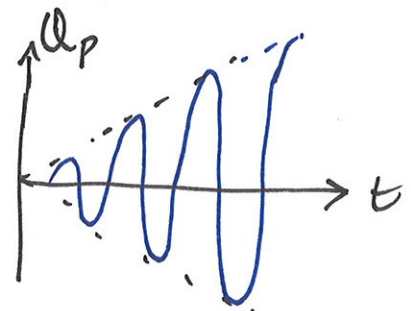
$$Q_p = \frac{A}{2L\omega} t \cdot \cos \beta t. \quad (\omega = \beta)$$



radio explodes???

Why doesn't this happen?

\rightarrow resistance in wires.

Instead :


$$LQ'' + RQ' + \frac{1}{C}Q = A \cos \beta t.$$

$$R > 0$$

Assume small resistance, $R < \sqrt{\frac{4L}{C}}$.

(no critical or overdamping).

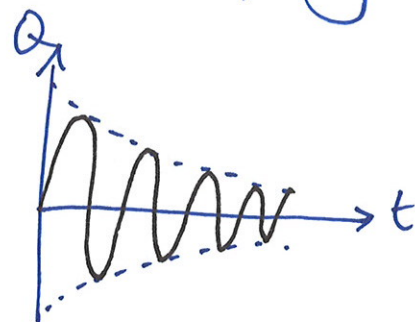Homogeneous solution
→ damped oscillations



(prove for yourself!)

Particular Solution:

$$Q_p = \frac{A\beta R}{L^2[(\omega^2 - \beta^2)^2 + (\frac{\beta R}{L})^2]} \sin(\beta t)$$

$$+ \frac{A(\omega^2 - \beta^2)}{L[(\omega^2 - \beta^2)^2 + (\frac{\beta R}{L})^2]} \cos(\beta t)$$

$$\omega = \frac{1}{\sqrt{CL}}$$


"natural
freq."

(undetermined coefs or
variation of parameters).

OR

$$Q_p = \frac{A}{L \sqrt{(\omega^2 - \beta^2)^2 + \left(\frac{\beta R}{L}\right)^2}} \cos\left\{\beta t - \tan^{-1}\left(\frac{\beta R}{L(\omega^2 - \beta^2)}\right)\right\}$$

amplitude of oscillations

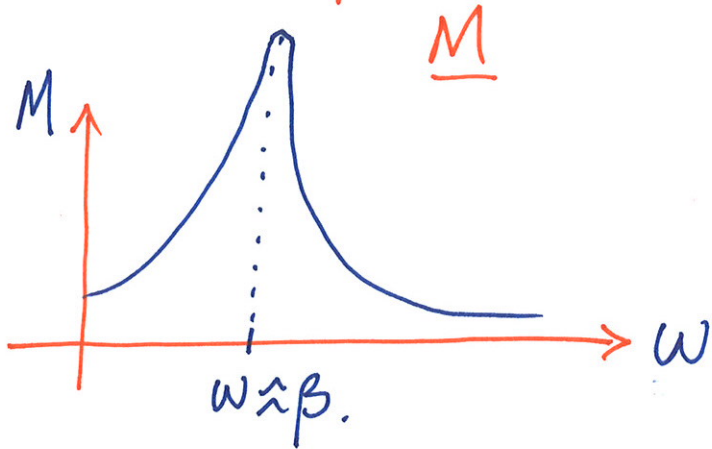

Amplified.
only
(maximized
amplitude of
oscs by tuning
natural freq. ω
to forcing freq. β
 \Rightarrow exploit
RESONANCE)

So what if we have multiple inputs?

$$LQ'' + RQ' + \frac{1}{C}Q = \sum_{n=1}^{\infty} A_n \cos(\beta_n t)$$

What if I want my radio to pick up
info. carried on freq. β_3 only?

$$Q_p = \sum_{n=1}^N \frac{A_n}{L \sqrt{(\omega^2 - \beta_n^2)^2 + \left(\frac{\beta_n R}{L}\right)^2}} \cos \left\{ \beta_n t - \tan^{-1} \left[\frac{\beta_n R}{L(\omega^2 - \beta_n^2)} \right] \right\}$$

want coeff. of $\cos \left\{ \beta_3 t - \tan^{-1} \left[\frac{\beta_3 R}{L(\omega^2 - \beta_3^2)} \right] \right\}$
to be big.

i.e.
$$\frac{A_3}{L \sqrt{(\omega^2 - \beta_3^2)^2 + \left(\frac{\beta_3 R}{L}\right)^2}}$$

⇒ ~~From~~ Tune radio by changing capacitance so $\omega = \frac{1}{\sqrt{CL}} \approx \beta_3$
